

Assignment–7

DESIGN OF OPAMP FOR MATHEMATICAL OPERATION

ee25btech11226 – Phani Vishnu Sree

ee25btech11011 – B. Navya


AIM


To design an operational amplifier circuit that performs the mathematical operation

$$V_o = 2V_1 - 3V_2$$

and test it using a DC source and a low frequency sinusoidal signal.

CIRCUIT

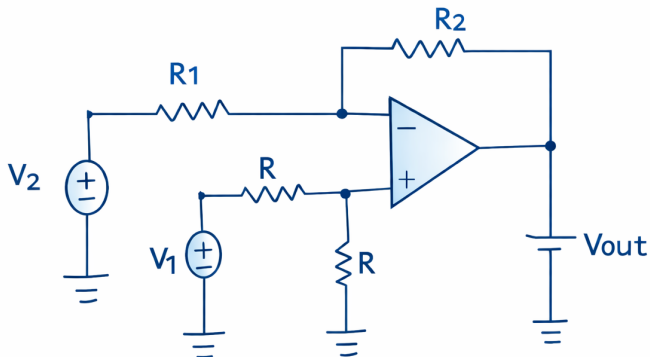

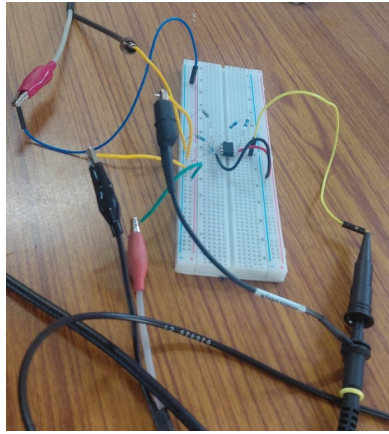

DERIVATION

From the input network,

$$V_1 - iR - iR = 0 \Rightarrow i = \frac{V_1}{2R}$$

Voltage at non-inverting terminal:

$$V_+ = V_1 - iR = V_1 - \frac{V_1}{2} = \frac{V_1}{2}$$

Using virtual short:

$$V_- = V_+ = \frac{V_1}{2}$$

Applying KCL at inverting node,

$$\begin{aligned} \frac{V_2 - \frac{V_1}{2}}{R_1} &= \frac{\frac{V_1}{2} - V_{out}}{R_2} \\ \Rightarrow V_{out} &= \frac{R_1 + R_2}{2R_1} V_1 - \frac{R_2}{R_1} V_2 \end{aligned}$$

For required operation $V_{out} = 2V_1 - 3V_2$,

$$\frac{R_1 + R_2}{2R_1} = 2, \quad \frac{R_2}{R_1} = 3$$

$$\Rightarrow R_2 = 3R_1$$

$$\frac{R_2}{R_1} = 3$$

To satisfy this condition, the following practical resistor values were used in the circuit:

- $R_1 = 10\text{ k}\Omega$
- $R_2 = 30\text{ k}\Omega$
- $R = 1\text{ k}\Omega$

Since a single $30\text{ k}\Omega$ resistor was not available, it was implemented by connecting two $15\text{ k}\Omega$ resistors in series

TESTING USING DC SOURCE

To verify the designed Op-Amp circuit for the operation


$$V_o = 2V_1 - 3V_2$$


DC voltages were applied as inputs V_1 and V_2 . The output voltage V_o was measured using an oscilloscope. Different combinations of input voltages were applied to verify the required operation.

For the applied DC input values:

1. When $V_1 = 1\text{ V}$ and $V_2 = 1\text{ V}$




$$V_o = 2(1) - 3(1) = -1\text{ V}$$

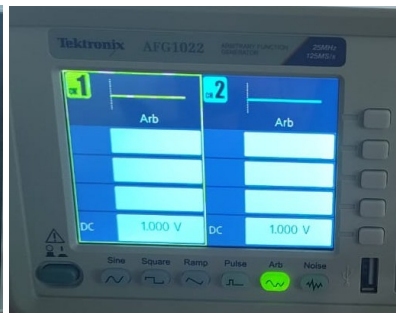

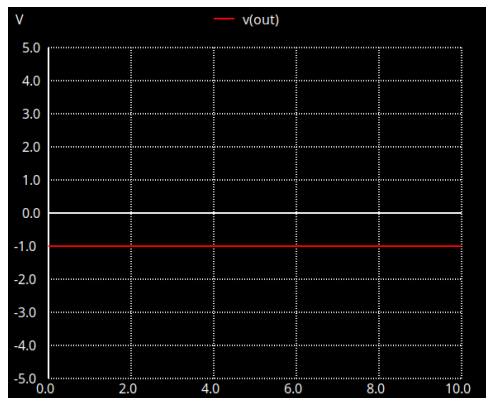



2. When $V_1 = 2\text{ V}$ and $V_2 = 2\text{ V}$

$$V_o = 2(2) - 3(2) = -2\text{ V}$$

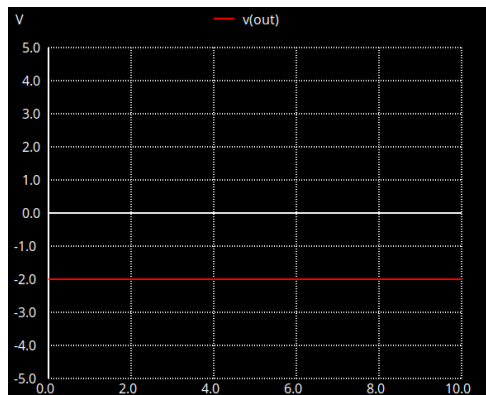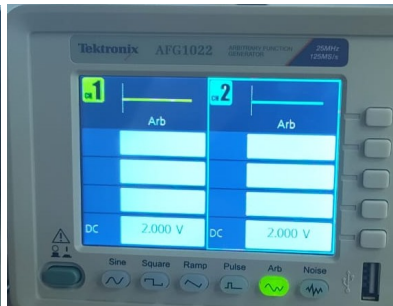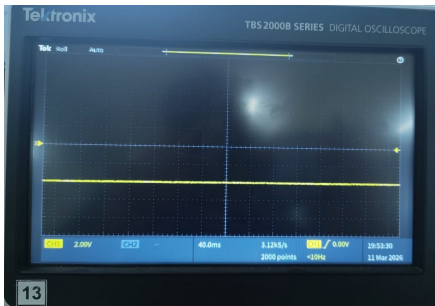

3. When $V_1 = 2\text{ V}$ and $V_2 = 1\text{ V}$

$$V_o = 2(2) - 3(1) = 1\text{ V}$$

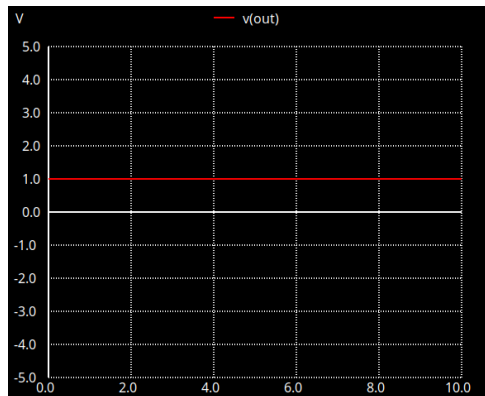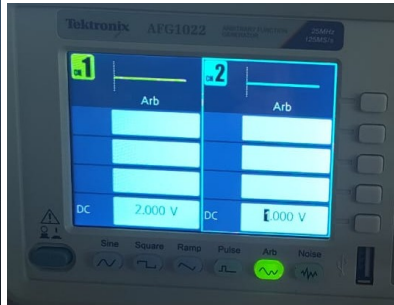

The measured output voltages matched the theoretical values, confirming that the Op-Amp circuit successfully performs the required operation.

TESTING USING LOW FREQUENCY SINUSOIDAL SIGNAL

The Op-Amp circuit was tested using low frequency sinusoidal signals applied to V_1 and V_2 using a function generator. The output was observed on a digital oscilloscope. A single output waveform was observed, which follows the relation

$$V_o = 2V_1 - 3V_2$$

This verifies that the circuit performs the required operation correctly.

